Task 1: Data Rep. and Boolean logic


Save this document in your repository for Unit 2 with name: data_rep_boolean_log.md


Resources (Learning Log):


4	Notes Topic 2:	Computer Architecture
5	Boolean Algebra	Video about boolean algebra
6	Examples Base Conversion	Whiteboard notes on conversion of numbers with different bases

Boolean Logic

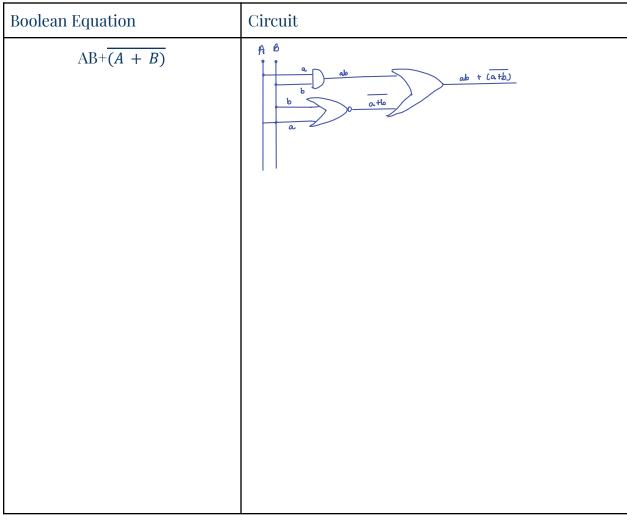Draw the circuit for the boolean equations provided




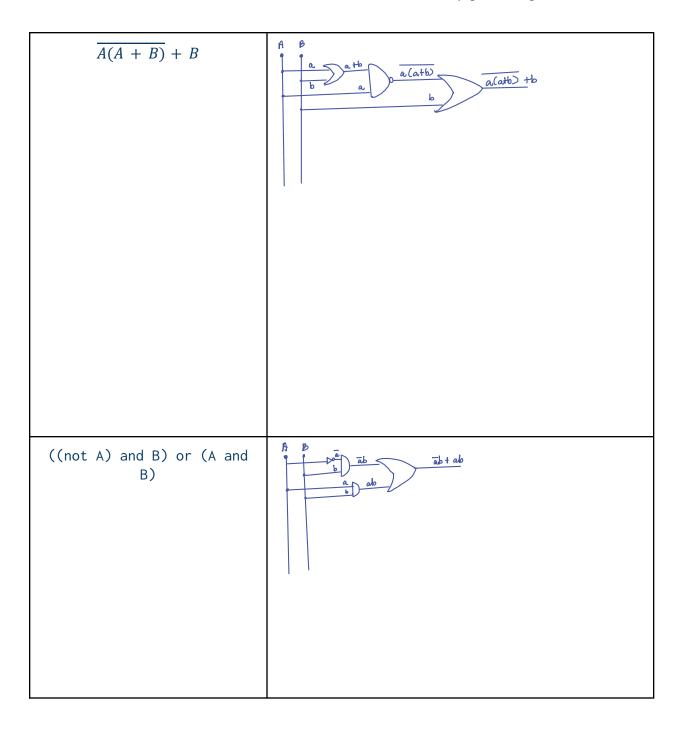


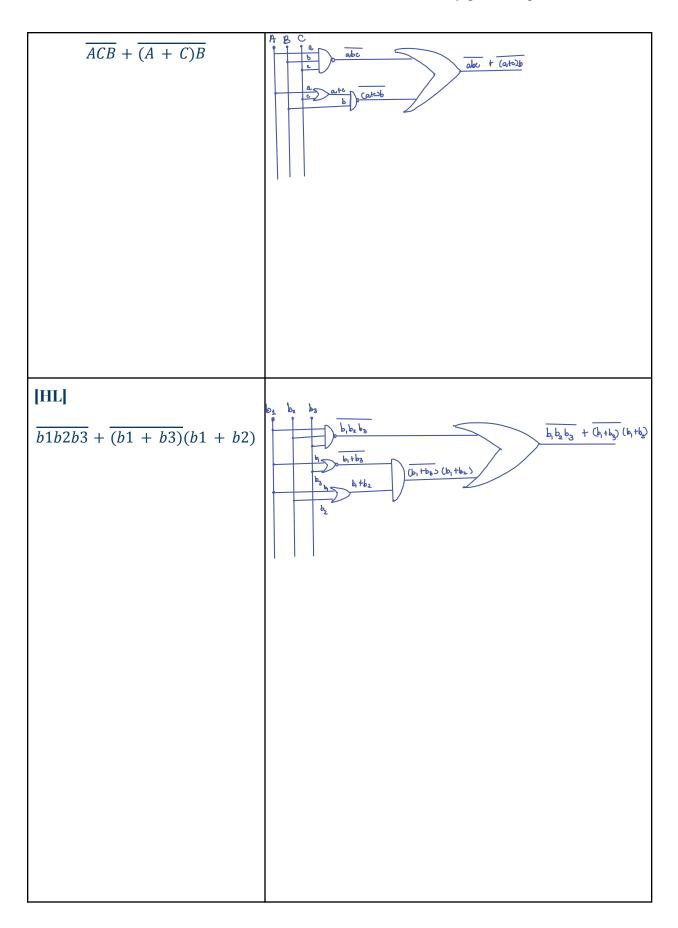

Get the Equation

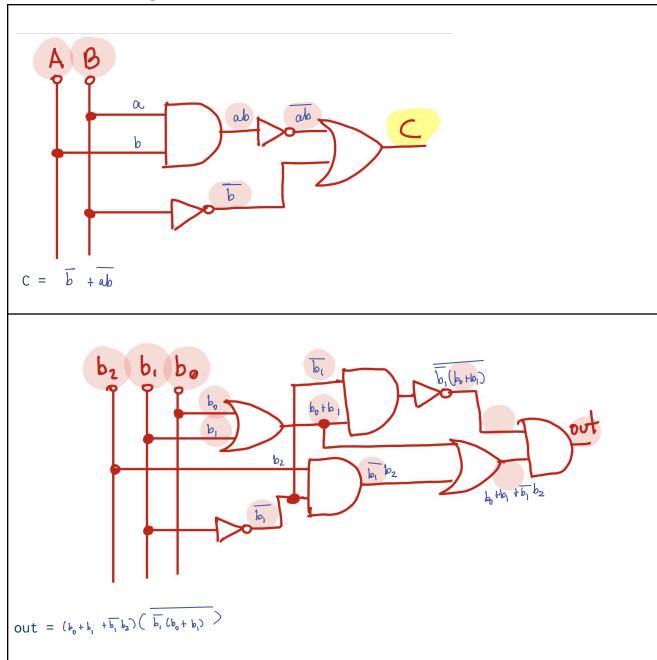Write the boolean equation for the circuit shown



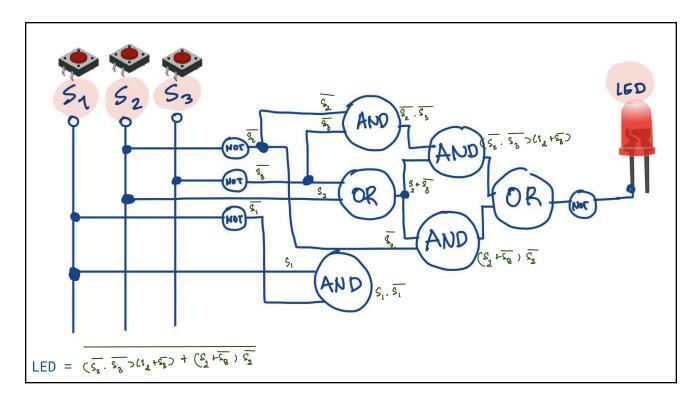

Truth table

W

127

(37

(A)

(5)

Write the truth table for the equations below

Boolean Equation	Truth Table
X = A and B	No
Out = input1 or input2	î ₁ + ì ₂
$Light = \overline{S_1} + \overline{(S_2 + S_3)} + S_1 S_2 \overline{S_3}$	
$PARITY = A \oplus B \oplus C$	#Parity checker
[HL] $Login = \overline{P_1 P_2 P_3} + \overline{(P_3 \overline{P_2 P_1})} + \overline{P_1 + P_3}$	

Data Conversion

Information can be represented in different systems, for example the number 10 in decimal (system base 10) can be represented in binary (system base 2) as 1010 or 12 in base 8.

It is critical for you to understand how to represent information in different ways, this will help you visualize how the computer processes data.


Take the remainder and read from bottom to top.

Binary - Decimal: write a table with base process of available related to a figure lase is at a divide If your base is dⁿ - divide

binary into something practs - multiple-add

UWC ISAK Japan Computer Science 2022

Original Number	Convert to
256 (Decimal) Bake to	Base 2 (Binary) $266 = 2^8 \rightarrow 100000000000000000000000000000000000$
433 (Base 5)	Base 10 (Decimal) west from base $\frac{1}{2}$ Decimal 1 Deau table a Normal $\frac{1}{2}$ \frac
FA32 (Base 16)	Base 10 256 163 164 164 165 164 165 266 164 204 204 204 204 204 204 204 2

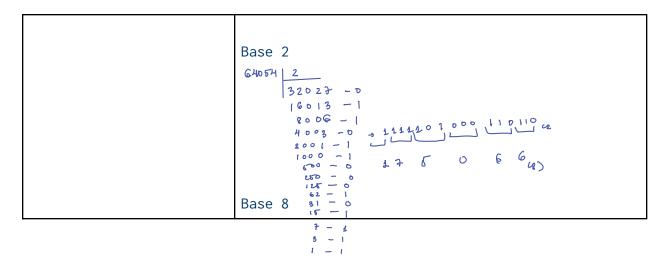

Touth Table:

Immin		40				. 0	
<u>(1)</u>	ع' ه	b	ou (alo)	2	a' input	in Int	out (iz+iz
	0	0	0		0	0	0
	O	1	0		O	1	Ŧ
	1	0	D 1		1	0	T
	1	1	1		1	7	7

3	2 ² S,	عا ا ا	S 3	<u>s</u>	Sats	S, S2 S3	dignt
	D	0	0	T	1	1	1
	D	O	1	1	0	1	4
	0	1	O	Ł	0	1	1
	0	1	1	1	0	7	1
	1	D	σ	٥	1	1	4
	4	O	ι	0	D	1	1
	4	Y	ь	D	D	7	エ
	1	1	1	0	D	0	0
			'	'	•		

4	22	ಎ¹	బ్		
	A	Ъ	ပ	A D	Panity
	D	0	0	0	b
	D	O	4	0	7
	0	1	0	1	4
	0	1	1	1	0
	1	D	0	1	1
	4	O	ι	1	0
	1	7.	b 1	0	<u>1</u>
				l	

(E) 22	ಎ¹	ఖ్	l i		ı 	ı ——	l
PL	اء	Ρ,	P, Pz Pz	P2P1	(P3 P2 P1)	P1+13	Login
D	0	0	1	£	Ŧ	4	1
P	O	1	1	1	0	t	1
0	1	0	(1	1	1	1
0	1	1	ι ,	1	Đ	0	1
1	D	0	Λ	1	4	D	1
4	0	ι	1	1	D	D	1
4	Y	b	1	1_	3_	D	1
1	7	1	0	О	1	D	7



Exit Ticket 1